

(Analog Output) - (PWM Pins)


2*Connecting Led on Arduino:

PWM Pins are special one that can get analog output . they devide the digital values (0,5) to 256 layers so , the can give values between 0 and 5 according to these 256 layers that starts from 0 to 255 the PWM pins are (3,5,6,9,10,11)


Algorithm:

the led brightness will be increased gradually til the maximum value and then be decreased till the minimum value

schematic:

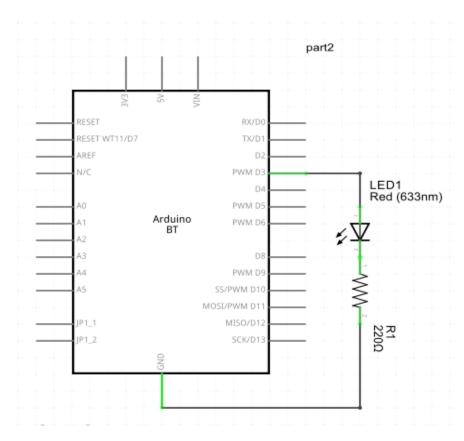


ON Arduino:

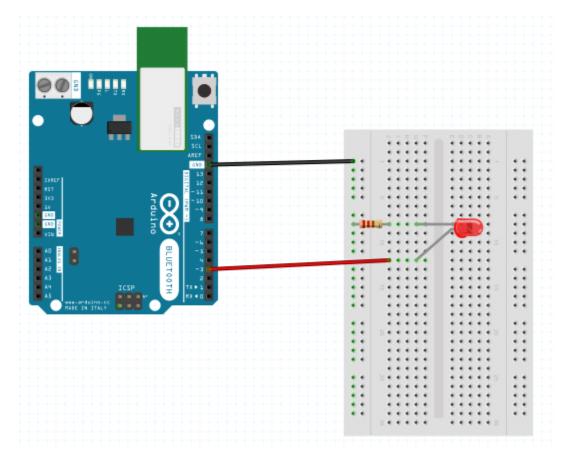

the code:

File Edit Sketch Tools Help

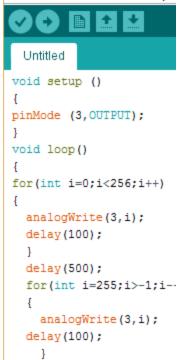

Done compiling.

}

delay(500);